

EE23BTECH11054 - Sai Krishna Shanigarapu*

GATE EE 2022

28. The network shown below has a resonant frequency of 150 kHz and bandwidth of 600 Hz. The Q-factor of the network is ____ (rounded off to one decimal place). (GATE 2022 EC)

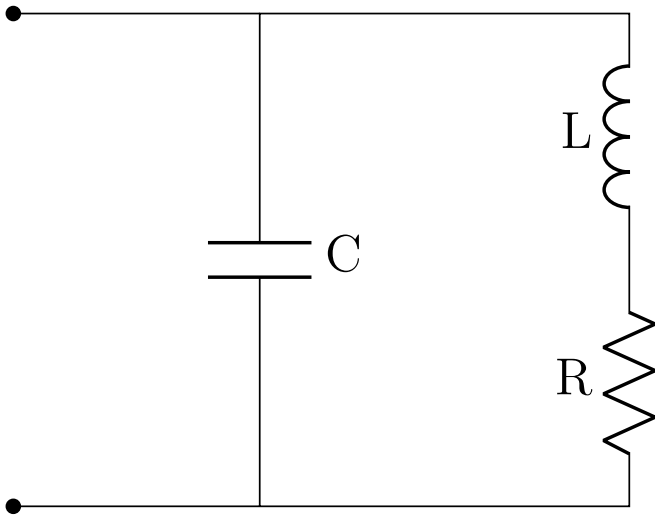


Fig. 1. Circuit 1

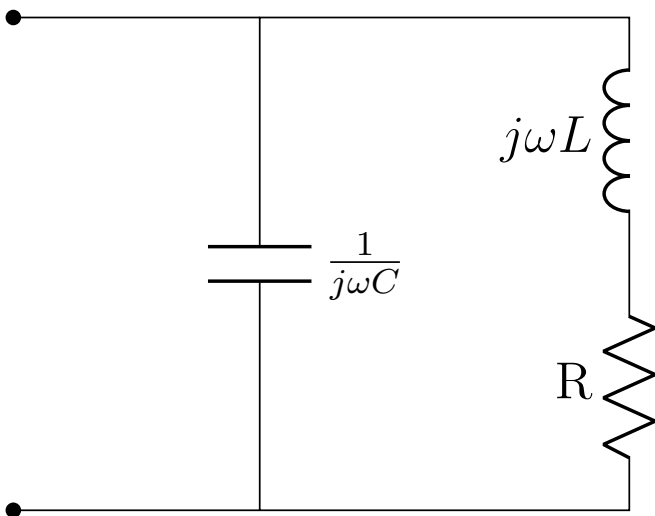
Solution:

Fig. 2. Circuit 2

Parameter	Description	Value
f_0	Resonant frequency	150 kHz
B	Bandwidth	600 Hz

TABLE I
PARAMETERS

Parameter	Description	Formula
Q	Quality factor	$\frac{X_L}{R}$
B	Bandwidth	$\frac{R}{2\pi L}$
ω_0	Radial resonant frequency	$2\pi f_0$
X_L	Inductive reactance	ωL
X_C	Capacitive reactance	$\frac{1}{\omega C}$

TABLE II
FORMULAE

At Resonance,

$$X_L = X_C \quad (1)$$

$$\omega_0 L = \frac{1}{\omega_0 C} \quad (2)$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (3)$$

$$2\pi f_0 = \frac{1}{\sqrt{LC}} \quad (4)$$

$$\Rightarrow f_0 = \frac{1}{2\pi \sqrt{LC}} \quad (5)$$

Using Table II,

$$Q = \frac{X_L}{R} \quad (6)$$

$$= \frac{\omega_0 L}{R} \quad (7)$$

$$= \left(\frac{1}{\sqrt{LC}} \right) \frac{L}{R} \quad (8)$$

$$\Rightarrow Q = \frac{1}{R} \sqrt{\frac{L}{C}} \quad (9)$$

From eq (5) and Table II

$$\frac{f_0}{B} = \left(\frac{1}{2\pi \sqrt{LC}} \right) \frac{2\pi L}{R} \quad (10)$$

$$= \left(\frac{1}{\sqrt{LC}} \right) \frac{L}{R} \quad (11)$$

$$\Rightarrow \frac{f_0}{B} = \frac{1}{R} \sqrt{\frac{L}{C}} \quad (12)$$

From Table I, eq (9) and eq (12),

$$Q = \frac{f_0}{B} \quad (13)$$

$$= \frac{150 \times 10^3}{600} \quad (14)$$

$$= 250 \quad (15)$$

\therefore Q-factor is 250

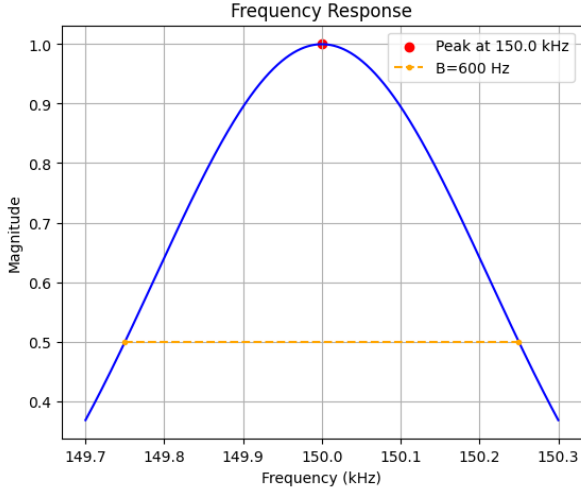


Fig. 3. Plot of Q-factor